
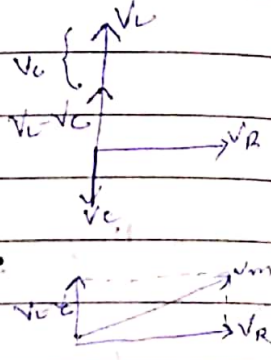



Date / /

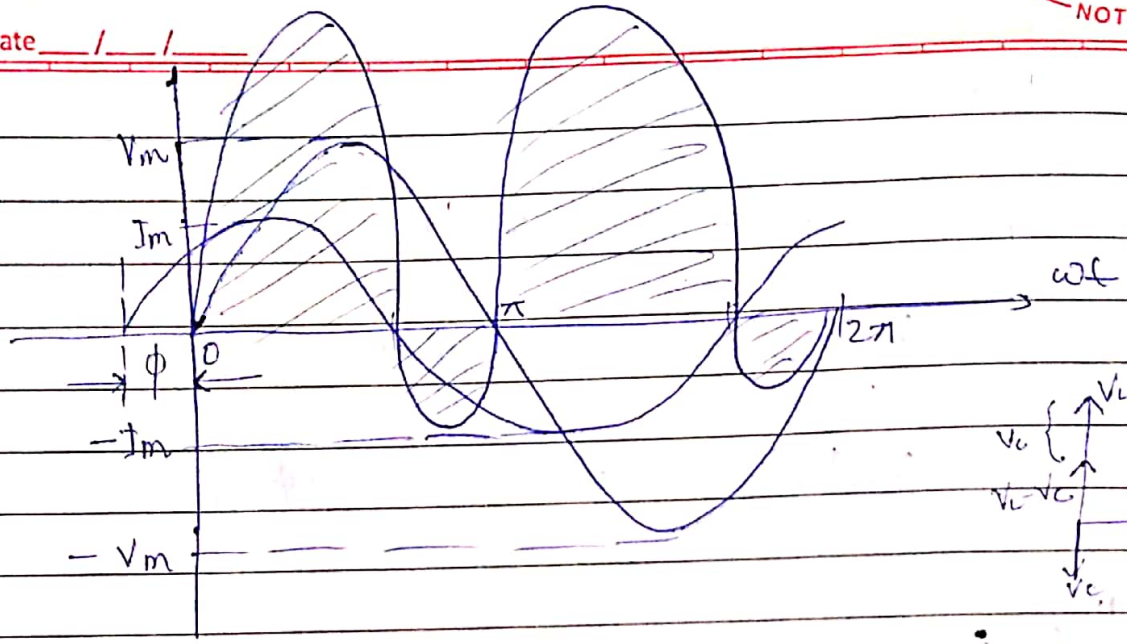$V = V_m \sin \omega t$
 $I = I_m \sin(\omega t - \phi)$




LCR series circuit

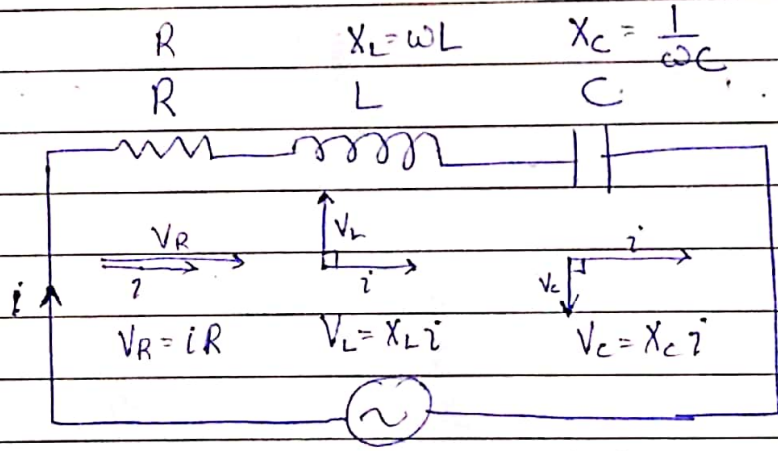$Z = \sqrt{R^2 + (X_L - X_C)^2}$
 $I = \frac{V}{Z}$



$V = V_m \sin \omega t$

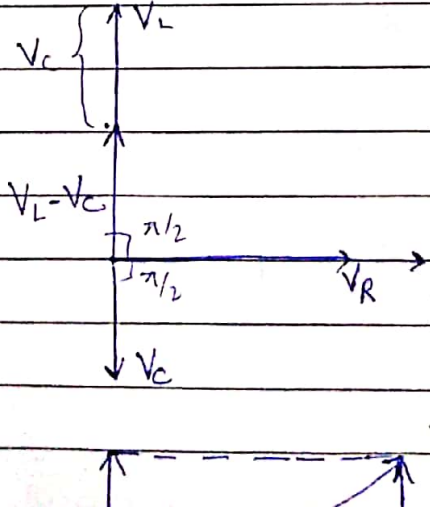

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \frac{V_m}{I_m}$$

$$I_m = \frac{V_m}{Z}$$

unit of $Z = \text{ohm} \cdot \Omega$

if $Z \downarrow \rightarrow I_m \uparrow$
 $Z \uparrow \rightarrow I_m \downarrow$

$$i = i_m \sin(\omega t \pm \phi)$$

$$v = V_m \sin \omega t$$

$$\cos \phi = \frac{R}{Z}$$

$$\cos \phi = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

Case 1

(i) $X_L > X_C$ RL

$$\phi = +ve$$

$$i = i_m \sin(\omega t - \phi)$$

(ii) $X_C > X_L$ RC

$$\phi = -ve$$


$$i = i_m \sin(\omega t + \phi)$$


(iii) $X_L = X_C$

$$\phi = 0$$

$$i = i_m \sin \omega t$$

purely
resistive

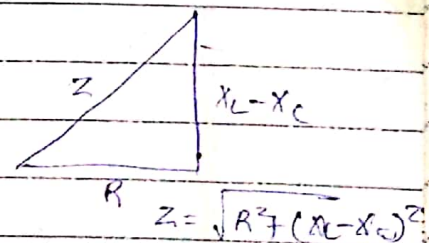

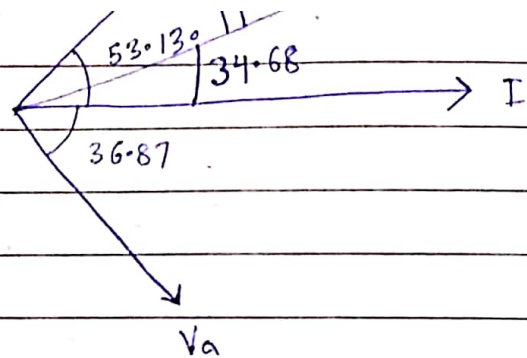

Single phase A.C. 11el circuit


Admittance (Y)

The Y of an A.C. circuit is defined as the reciprocal of its Impedance i.e. admittance $Y = \frac{1}{Z} = \frac{1}{V/I} = \frac{I}{V}$
unit - Siemen (S)

$$Z = R + jX_L$$

$$Z = R - jX_C$$

when R & L are in 11el

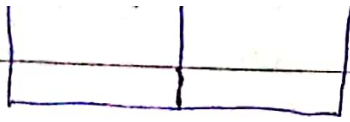

Apply KCL


$$I = I_1 + I_2$$

$$\frac{V}{Z} = \frac{V}{R} + \frac{V}{jX_L}$$

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{jX_L}$$

$$Y = G - jB_L \quad \text{Inductive substance}$$

R & C in parallel

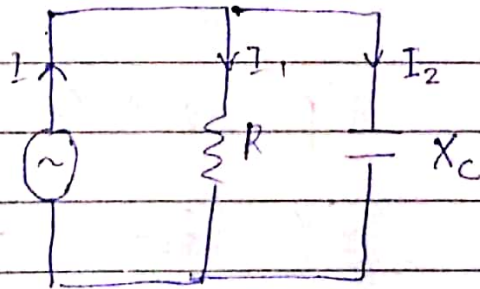

Apply KCL

$$I = I_1 + I_2$$

$$\frac{V}{Z} = \frac{V}{R} + \frac{V}{-jX_C}$$

$$Y = G + jB_C$$

$$\phi = \tan^{-1} \left[\frac{B}{G} \right]$$

In general


$$Y = G \pm jB$$

Concept.


$$V_{\text{stat}} = \frac{1}{2} \sum_k W_k \left[\omega_k^2 v_k^2 - (\omega_k v_k) \right]$$

Date / /

Unirite
NOTEBOOK

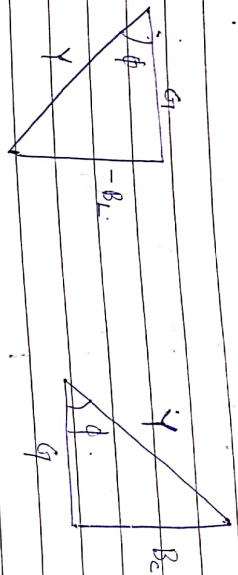

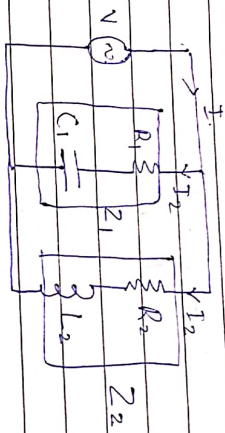q. Find general eqn of Y Admittance matrix for 11kV AC System




$$Z_1 = R_1 - jX_{C_1} \quad Y_1 = G_1 + jB_1$$

$$Z_2 = R_2 + jX_{L_2} \quad Y_2 = G_2 - jB_2$$


$$Y = Y_1 + Y_2$$

$$Y = (G_1 + G_2) + j(B_1 - B_2)$$
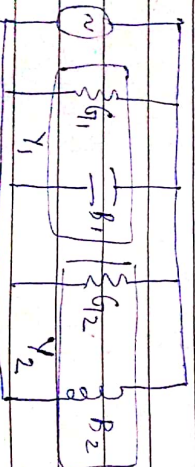
$$Y = G + jB \quad \text{--- General equation}$$



Application of admittance method

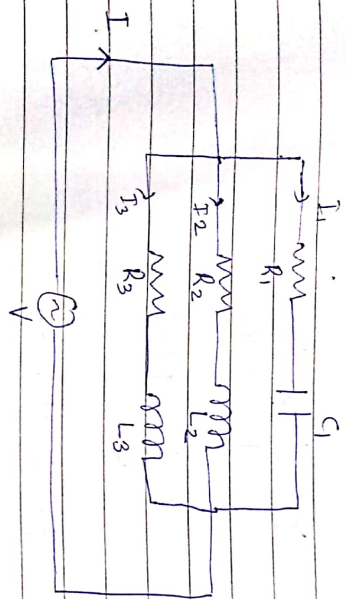

The magnitudes of various circuit values are

(1) Total conductance $(G) = G_1 + G_2 + G_3$

(2) Total susceptance $(B) = B_1 - B_2 - B_3$

(3) Magnitude of admittance $Y = \sqrt{G^2 + B^2}$

(4) Total current I in terms of $Y = VY$

(5) Power factor $(\cos \phi) = G/Y$

(6) Power consumed $P = VI \cos \phi$
 $= V^2 G$

(7) Branch current $I_1 = VY_1$

(8) Phase angle $\phi = \tan^{-1} \left[\frac{B}{G} \right]$

$\phi = +ve$ leads

$\phi = -ve$ lags

R & C in parallel

$$Y = \frac{1}{R} + \frac{1}{-jX_C}$$

$$Y = \frac{1}{R} + j\omega C$$

$$\phi = \tan^{-1}(\omega C R)$$

$$|Y| = \sqrt{\left(\frac{1}{R}\right)^2 + (\omega C)^2}$$

R & L in parallel

$$Y = \frac{1}{R} + \frac{1}{jX_L}$$

$$Y = \frac{1}{R} + \left(\frac{-j}{\omega L} \right)$$

$$\phi = \tan^{-1} \left[\frac{-1 \times R}{\omega L} \right]$$

$$= \tan^{-1} \left[\frac{R}{\omega L} \right]$$

$$|Y| = \sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{\omega L}\right)^2}$$

$$\text{form factor} = \frac{\text{RMS value}}{\text{Avg. value}}$$

$$= \frac{I_m}{(\sqrt{2})^2} \times \frac{\pi}{I_m}$$

$$\boxed{\text{form factor} = \frac{\pi}{2}}$$

$$\boxed{\text{peak factor} = \frac{\text{Max. value}}{\text{RMS value}} = \frac{I_m}{I_m} \times \frac{2}{\sqrt{2}} = 2}$$

(ii) $I_{avg} = \frac{\text{area under wf over full cycle}}{\text{period of the cycle.}}$

$$= \frac{1}{\pi} \int_0^{\pi} I_m \sin \omega t \, d(\omega t)$$

$$= \frac{I_m}{\pi} \int_0^{\pi} \sin \omega t \, d(\omega t)$$

$$= \frac{I_m}{\pi} [-\cos \omega t]_0^{\pi}$$

$$= \frac{I_m}{\pi} [-\cos \pi - (-\cos 0)]$$

$$= \frac{I_m}{\pi} \times [1 + 1]$$


$$\boxed{I_{avg} = \frac{2 I_m}{\pi}}$$

$$P.f. = \frac{I_m \times \sqrt{2}}{I_m}$$

$$\boxed{P.f. = \sqrt{2}}$$

$$\text{form factor} = \frac{I_m}{\sqrt{2}} \times \frac{\pi}{2 I_m}$$

$$\boxed{P.f. = \frac{\pi}{2\sqrt{2}}}$$

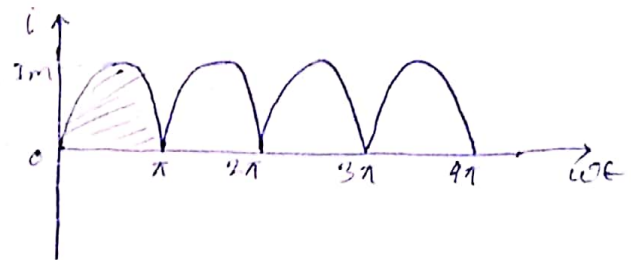

$$I_{rms} = \sqrt{\frac{\text{area of square wf over full cycle}}{\text{period the full wave cycle}}}$$

$$= \sqrt{\frac{\int_0^{\pi} I_m^2 \sin^2 \omega t \, d(\omega t)}{\pi}}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \int_0^{\pi} (2 \sin^2 \omega t) \, d(\omega t)}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \int_0^{\pi} (1 - \cos 2\omega t) \, d(\omega t)}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \left[\omega t - \frac{\sin 2\omega t}{2} \right]_0^{\pi}}$$

$$= \left[\frac{I_m^2}{2\pi} \left(\pi - \frac{\sin 2\pi}{2} - 0 + \frac{\sin 2 \times 0}{2} \right) \right]^{\frac{1}{2}}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \times \pi} = \boxed{\frac{I_m}{\sqrt{2}} = I_{rms}}$$


Find the avg. value, RMS value, form factor and peak factor for

(i) Half wave rectified AC

(ii) Full wave " AC

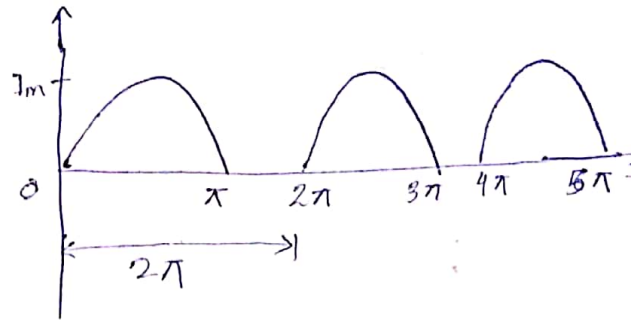(i) $I_{avg} = \frac{\text{area under w.f over full cycle}}{\text{Period of the waveform}}$

$$= \frac{\int_0^{\pi} I_m \sin \omega t \, d(\omega t)}{2\pi}$$



$$= \frac{I_m}{2\pi} \left[-\cos \omega t \right]_0^{\pi} = \frac{I_m}{2\pi} \left[-\cos \pi - (-\cos 0) \right]$$

$$= \frac{I_m}{2\pi} \times 2 = \frac{I_m}{\pi}$$

$$\therefore I_{avg} = \frac{I_m}{\pi}$$


$$I_{rms} = \sqrt{\frac{\text{area of the square w.f over full cycle}}{\text{Period of the full cycle}}}$$

$$= \sqrt{\frac{\int_0^{\pi} I_m^2 \sin^2 \omega t \, d(\omega t)}{2\pi}}$$

$$= \sqrt{\frac{I_m^2 \int_0^{\pi} (1 - \cos 2\omega t) \, d(\omega t)}{4\pi}} = \sqrt{\frac{I_m^2}{4\pi} \left[\omega t - \frac{\sin 2\omega t}{2} \right]_0^{\pi}}$$

$$= \sqrt{\frac{I_m^2}{4\pi} [\pi - 0 - (0 - 0)]} = \sqrt{\frac{I_m^2}{4}} = \frac{I_m}{2}$$

$$\therefore I_{rms} = \frac{I_m}{2}$$

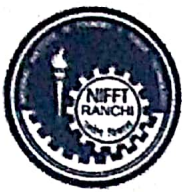

SHEET NO :


Determine rms and avg. value of waveform.

solⁿ As we know that

$$y = mx + c$$

$$y = \left(\frac{20-10}{T} \right) t + 10$$

$$y = \frac{10}{T} t + 10$$

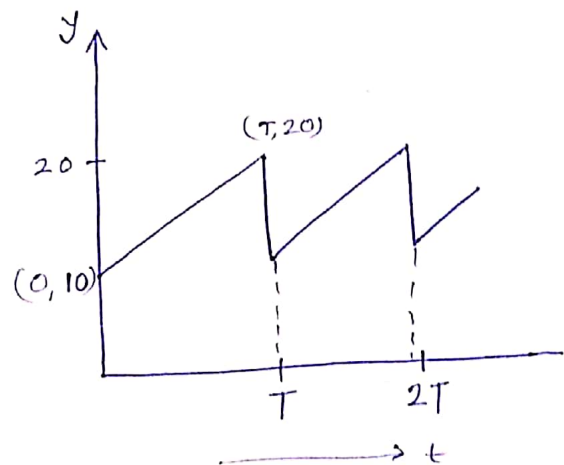

$$Y_{avg} = \frac{1}{T} \int_0^T \left(\frac{10t}{T} + 10 \right) dt$$

$$= \frac{1}{T} \left[\frac{10}{T} \times \left(\frac{t^2}{2} \right)_0^T + 10[t]_0^T \right]$$

$$= \frac{1}{T} \left[\frac{10}{T} \times \frac{T^2}{2} + 10T \right]$$

$$= \frac{1}{T} \left[\frac{10T + 20T}{2} \right]$$

$$Y_{avg} = 15$$

$$Y_{rms} = \sqrt{\frac{1}{T} \int_0^T y^2 dt}$$

$$= \int_0^T \left(\frac{100}{T^2} t^2 + 100 \right) dt$$

$$= \frac{100}{T^2} \times \frac{T^3}{3} + 100T$$

$$= \frac{100T + 300T}{3} = \frac{400T}{3}$$

$$Y_{rms} = \sqrt{\frac{1}{T} \times \frac{400T}{3}}$$

$$= \frac{20}{\sqrt{3}} = \frac{700}{3}$$

$$\therefore Y_{rms} = 15.2$$

For the trapezoidal current wave-form. Determine the effective value

when $0 < t < \frac{3T}{20}$

$$i = \frac{I_m}{3T} \times 20 \cdot t$$

$$i = \frac{20 I_m}{3T} \cdot t$$

when $\frac{3T}{20} < t < \frac{7T}{20}$

$$i = I_m$$

$$I_{avg} = \frac{1}{T/2} \left\{ 2 \int_0^{3T/20} i dt + \int_{3T/20}^{7T/20} I_m dt \right\}$$

$$= \frac{2}{T} \left\{ 2 \int_0^{3T/20} \left(\frac{20 I_m}{3T} \right) t dt + I_m \int_{3T/20}^{7T/20} dt \right\}$$


$$= \frac{2}{T} \left\{ 2 \left(\frac{20 I_m}{3T} \right) \left[\frac{t^2}{2} \right]_0^{3T/20} + I_m \left[t \right]_{3T/20}^{7T/20} \right\}$$

$$I_{avg} = \frac{7}{10} I_m$$

$$I_{rms} = \sqrt{\frac{1}{T/2} \left[2 \int_0^{3T/20} i^2 dt + \int_{3T/20}^{7T/20} I_m^2 dt \right]}$$

$$= \sqrt{\frac{2}{T} \left[2 \left(\frac{20 I_m}{3T} \right)^2 \int_0^{3T/20} t^2 dt + I_m^2 \int_{3T/20}^{7T/20} dt \right]} = \frac{3}{5} I_m$$
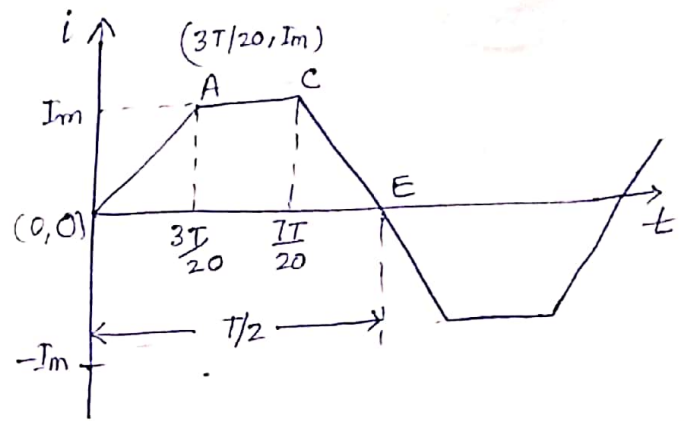
$$I = \sqrt{\left(\frac{3}{5} \right)} \cdot I_m = 0.775 I_m$$



$$i = \frac{I_m \times 20}{3T \times 1} \cdot t \quad \text{Rough}$$

$$i = \frac{I_m}{3T} 20t$$

$$i = \frac{20 I_m}{3T} t$$


Find the avg and effective values of voltage of sinusoidal waveform as shown.

$$V_{avg} = \frac{1}{2\pi} \int_{\pi/4}^{\pi} 100 \sin \theta d\theta$$

$$= \frac{100}{2\pi} \left[-\cos \theta \right]_{\pi/4}^{\pi}$$

$$= \frac{100}{2\pi} \left[-\cos \pi + \cos \pi/4 \right]$$
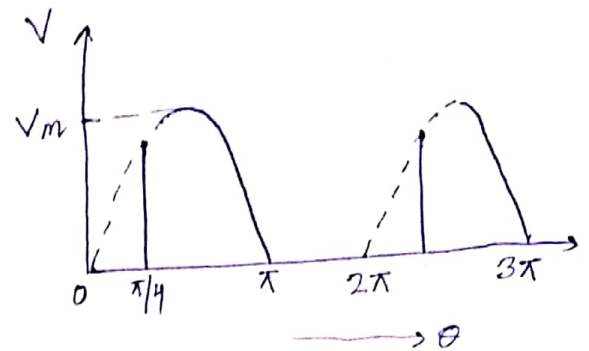
$$= \frac{100}{2\pi} \left[1 + 0.707 \right] = 27.2 \text{ V}$$



$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_{\pi/4}^{\pi} (100^2 \sin^2 \theta d\theta)}$$

$$= \sqrt{\frac{100^2}{4\pi} \int_{\pi/4}^{\pi} 2 \sin^2 \theta d\theta}$$

$$= \sqrt{\frac{100^2}{4\pi} \int_{\pi/4}^{\pi} (1 - \cos 2\theta) d\theta}$$

$$= \sqrt{\frac{100^2}{4\pi} \left[\theta - \frac{\sin 2\theta}{2} \right]_{\pi/4}^{\pi}}$$

$$= \sqrt{\frac{100^2}{4\pi} \left[\frac{\pi}{1} - \frac{\sin 2\pi}{2} - \frac{\pi}{4} + \frac{\sin \pi/2}{2} \right]}$$

$$= \sqrt{\frac{100^2}{4\pi} \left[\frac{\pi}{2} \right]}$$

$$\underline{V_{rms}} = \sqrt{\frac{25}{2\pi}} = 47.7 \text{ V}$$

Q. A delayed full wave rectified sinusoidal current has an avg. value equal to half its max. value. Find the delay angle θ

Given, $I_{avg} = \frac{I_m}{2}$

$$I_{avg} = \frac{1}{\pi} \int_{\theta}^{\pi} I_m \sin \theta \, d\theta$$

$$= \frac{I_m}{\pi} [-\cos \theta]_{\theta}^{\pi}$$

$$= \frac{I_m}{\pi} [-\cos \pi + \cos \theta]$$

It is given that,

$$I_{avg} = \frac{I_m}{2}$$

Now,

$$\frac{I_m}{2} = \frac{I_m}{\pi} [-\cos \pi + \cos \theta]$$

$$\frac{\pi}{2} - 1 = \cos \theta$$

$$\frac{\pi - 2}{2} = \cos \theta$$

$$\theta = \cos^{-1} \left(\frac{1.14}{2} \right)$$

$$\therefore \theta = 55.25^\circ$$

